


Measurements in a non-50 Ohm Universe (065)

Creating the Impedance Matching Pad

R_2 , the series resistor is equal to

$$R_2 = \sqrt{(R_{Hi-Z})^2 - [(R_{Lo-Z}) * (R_{Hi-Z})]}$$

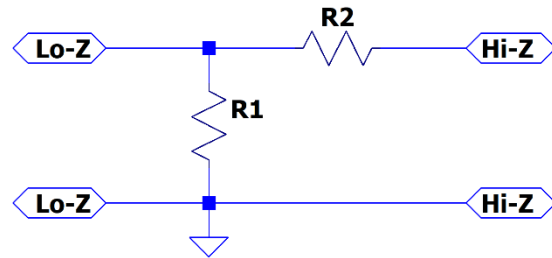Where R_{Hi-Z} is the high impedance side. In our case, this is 75 Ohms. And R_{Lo-Z} is the low impedance side. In our case here, this is 50 Ohms looking into the VNA.



This would give us an $R_2 = 43.3 \text{ Ohms}$. This is not a standard resistor value, but 43.2 Ohms is.

Now that we know what R_2 needs to be, we can calculate what the parallel resistor, R_1 needs to be.

$$R_1 = \frac{R_{Lo-Z} * (R_{Hi-Z} - R_2)}{R_{Lo-Z} - R_{Hi-Z} + R_2}$$

Plugging our value for R_2 into this equation, we get $R_1 = 86.6 \text{ Ohms}$. This is a standard resistor value.

Translating the 50 Ohm Measurement to the 75 Ohm Universe

Whatever the reported impedance is ... multiply it by the characteristic impedance of the world you are operating in and then divide by 50, the world of the VNA.

So, for instance ... at 25 MHz the reported input impedance of my filter is $53.744 - 9.5653j$.

This is in the 50 Ohm world of the VNA.

Let's translate this to the 75 Ohm world that my filter lives in ...

$$Z_{in}(75\Omega) = \frac{75}{50} * (Z_{in}(50\Omega))$$

$$Z_{in}(75\Omega) = \frac{75}{50} * (53.744 - 9.5653j)$$

$$= \frac{75}{50} * 53.744 - \frac{75}{50} * 9.5653j$$

$$Z_{in}(75\Omega) = 80.616 - 14.348j$$